

SCHOOL OF ELECTRONICS ENGINEERING
KALINGA INSTITUTE OF INDUSTRIAL TECHNOLOGY (KIIT)



VLSI LABORATORY REPORT
(EC-3095)

Submitted By

Name: Debagnik Kar

Roll No: 1804373

Section: ETC-06

Semester: 6th semester

Experiment: 5th

Design of traffic light controller using verilog and it's FPGA implementation.

Experiment -06


Aim: Design of traffic light controller using verilog and its FPGA implementation.

Software Used: EDA playground.


Theory:-

Traffic lights are signaling devices positioned at pedestrian crossing road, intersections, and other locations to control the flow of traffic. It allocates the right of way to road users using lights in standard colours (Red - yellow - green). It is often useful to be able to sequence through an arbitrary number of states, staying in each through an arbitrary number of amount of time.

• Four way Traffic light

 

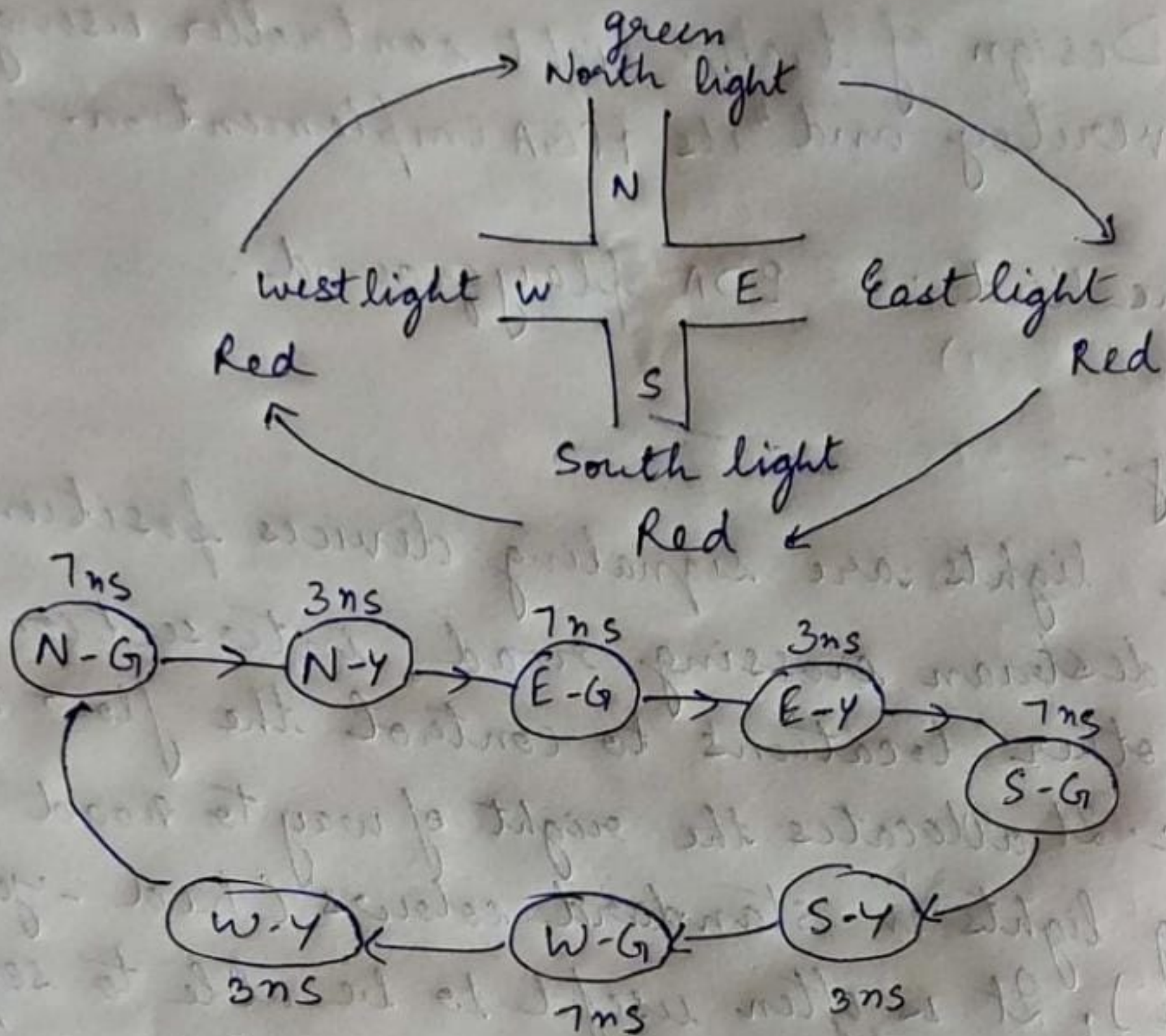In this system if one way is green/yellow others are red.



There are 8 parameters, so $[2:0]$ states

Initially, all 4 signals are kept red. Each signal will change the state after 10nsec. First the north becomes green for 7ns and yellow for next 3ns. Simultaneously, all the other 3 signals will perform the above same in next 10 sec.

Code:

Design.sv

```
module traffic_light(output [2:0] north,east,south,west, input clock,reset);
    reg [2:0] north,east,south,west;
    reg [2:0] state;
    reg [2:0] count;
    parameter n_g = 3'b000,n_y = 3'b001,e_g = 3'b010,e_y = 3'b011,s_g = 3'b100,s_y =
3'b101,w_g = 3'b110,w_y = 3'b111;
    parameter red = 3'b100, yellow = 3'b010, green = 3'b001;
    always @(posedge clock or posedge reset) begin
        if(reset) begin
            count=0;
            state=n_g;
        end
        else if(count==7) begin
            case(state)
                n_g: begin state=n_y; count=0; end
                e_g: begin state=e_y; count=0; end
                s_g: begin state=s_y; count=0; end
                w_g: begin state=w_y; count=0; end
                //default: begin state=n_y; count=0; end
            endcase
        end
        else if(count==3) begin
            case(state)
                n_y: begin state=e_g; count=0; end
                e_y: begin state=s_g; count=0; end
                s_y: begin state=w_g; count=0; end
                w_y: begin state=n_g; count=0; end
            endcase
        end
        count=count+1;
    end
    always@(state) begin
        case(state)
            n_g: begin north=green; east=red; south=red; west=red; end
            n_y: begin north=yellow; east=red; south=red; west=red; end
            e_g: begin north=red; east=green; south=red; west=red; end
            e_y: begin north=red; east=yellow; south=red; west=red; end
            s_g: begin north=red; east=red; south=green; west=red; end
            s_y: begin north=red; east=red; south=yellow; west=red; end
            w_g: begin north=red; east=red; south=red; west=green; end
            w_y: begin north=red; east=red; south=red; west=yellow; end
            default: begin north=green; east=red; south=red; west=red; end
        endcase
    end
endmodule
```


Testbench.sv

```
// Code your testbench here
// or browse Examples
module traffic_light_test;
    reg clock,reset;
    wire [2:0] north,east,south,west;
    traffic_light tt(north,east,south,west,clock,reset);
    always #10 clock=!clock;
    initial begin
        $dumpfile("dump.vcd"); $dumpvars;
        clock=0;reset=1;
        #10 reset=0;
    end
endmodule
```

Observation/outputs:



Fig 1: output

Conclusion

In this experiment we have successfully designed the 4 way traffic light controller on EDA playground by writing the code and also simulated it to obtain the required waveform and observed the output.