

**SCHOOL OF ELECTRONICS ENGINEERING**  
**KALINGA INSTITUTE OF INDUSTRIAL TECHNOLOGY (KIIT)**



**VLSI LABORATORY REPORT**  
**(EC-3095)**

**Submitted By**

**Name:** Debagnik Kar

**Roll No:** 1804373

**Section:** ETC-06

**Semester:** 6<sup>th</sup> semester

**Experiment:** 5<sup>th</sup>

Mealy and moore machines

## Experiment No - 05

Aim: (i) Modeling finite state machine (FSM) in Verilog.

(ii) Design of sequence detector (overlapping and non-overlapping sequence) using Mealy FSM.

(iii) Design of sequence detector (overlapping and non-overlapping sequence) using Moore FSM.

Software Used: EDA playground

Theory :-

Finite State Machine (FSM) are sequential circuit used in many digital systems to control the behavior of systems and data flow paths. Examples of FSM include control units and sequencers. This experiment introduces the concept of two types of FSMs, Mealy and Moore, and the modeling styles to develop such machines. Please refer to the two types shown below.




## > Mealy Machine (FSM)

A sequence detector is a sequential state machine which takes an input string of bits and generates an output 1 whenever the target sequence has been detected. In an a Mealy machine, output depends on the present state and the external input ( $x$ ). Hence in the state diagram, the output is written outside the states, along with inputs.

Sequence detector is of two types:

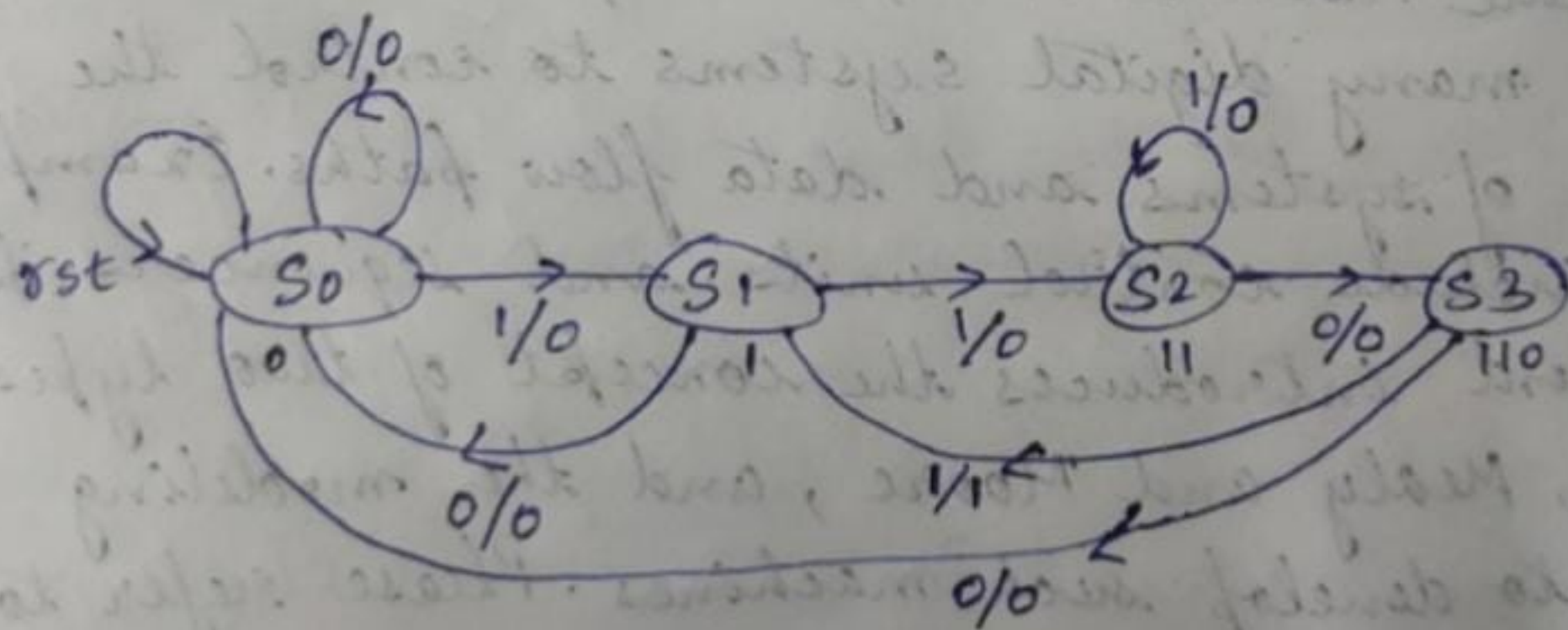1) Overlapping - In an overlapping sequence detector the last bit of one sequence becomes the first bit of next sequence. ~~However~~


\* Diagram of 1101 overlapping Mealy Model





2) Non-overlapping  $\rightarrow$  In non-overlapping sequence detector the last bit of one sequence does not become the first bit of next sequence.
 
# Diagram of 1101 non-overlapping Mealy Model



2) Moore Machine (FSM)

In moore machine, output depends only on the present state and not dependent on the input (x). Hence in the diagram output is written with the states. It has one more state than Mealy model and this also has two types of sequence detectors:-

1) overlapping

2) Non-overlapping



# Diagram of 1011 overlapping Moore Model

```

graph LR
    S0((S0/0)) -- 0 --> S0
    S0 -- 1 --> S1((S1/0))
    S1 -- 0 --> S1
    S1 -- 1 --> S2((S2/0))
    S2 -- 0 --> S2
    S2 -- 1 --> S3((S3/0))
    S3 -- 0 --> S3
    S3 -- 1 --> S4((S4/1))
    S4 -- 0 --> S0
    S4 -- 1 --> S2
    style S0 fill:#fff,stroke:#000
    style S1 fill:#fff,stroke:#000
    style S2 fill:#fff,stroke:#000
    style S3 fill:#fff,stroke:#000
    style S4 fill:#fff,stroke:#000
    
```

# Diagram of 1011 non-overlapping Moore Model

```

graph LR
    S0((S0/0)) -- 0 --> S0
    S0 -- 1 --> S1((S1/0))
    S1 -- 0 --> S1
    S1 -- 1 --> S2((S2/0))
    S2 -- 0 --> S0
    S2 -- 1 --> S3((S3/0))
    S3 -- 0 --> S0
    S3 -- 1 --> S4((S4/1))
    S4 -- 1 --> S0
    style S0 fill:#fff,stroke:#000
    style S1 fill:#fff,stroke:#000
    style S2 fill:#fff,stroke:#000
    style S3 fill:#fff,stroke:#000
    style S4 fill:#fff,stroke:#000
    
```

Debagnik Kar 1804373

# Code

## Moore machine

### Overlap method:

#### Design.sv

```
module moore_1011_overLAP(output dout,input din,clock,reset);
  reg dout;
  reg [2:0]state;
  parameter s0=3'b000,s1=3'b001,s2=3'b010,s3=3'b011,s4=3'b100;
  always@(posedge clock or posedge reset) begin
    if(reset) begin
      dout<=0;
      state<=s0;
    end
    else begin
      case(state)
        s0:begin dout<=0;
          if(din==1)
            state<=s1;
          else
            state<=s0;
          end
        s1:begin dout<=0;
          if(din==1)
            state<=s1;
          else
            state<=s2;
          end
        s2:begin dout<=0;
          if(din==1)
            state<=s3;
          else
            state<=s2;
          end
        s3:begin dout<=0;
          if(din==1)
            state<=s4;
          else
            state<=s2;
          end
        s4:begin dout<=1;
          if(din==1)
            state<=s1;
          else
            state<=s2;
          end
        default:begin dout<=0;state<=s0;end
      endcase
    end
  end
```

```
end
endmodule
```

### **Testbench.sv**

```
module moore_1011_overLAP_test;
  reg din, reset, clock;
  wire dout;
  moore_1011_overLAP m1(dout,din,clock,reset);
  always #10 clock=!clock;
  initial begin
    $dumpfile("dump.vcd"); $dumpvars;
    clock=0;
    reset=1;
    din=1;
    #20 reset=0;din=0;
    #20 din=1;
    #20 din=0;
    #20 din=1;
    #20 din=1;
    #20 din=0;
    #20 din=1;
    #20 din=0;
    #20 din=1;
    #20 din=1;
    #20 din=0;
    #20 din=1;
    #20 din=1;
    #20 din=0;
    #20 din=1;
    #20 din=0;
    end
endmodule
```

### **Non-overlap Method**

#### **Design.sv**

```
module moore_1011_non_overLAP(output dout,input din,clock,reset);
  reg dout;
  reg [2:0]state;
  parameter s0=3'b000,s1=3'b001,s2=3'b010,s3=3'b011,s4=3'b100;
  always@(posedge clock or posedge reset) begin
    if(reset) begin
      dout<=0;
      state<=s0;
    end
    else begin
      case(state)
```

```

s0:begin dout<=0;
if(din==1)
state<=s1;
else
state<=s0;
end
s1:begin dout<=0;
if(din==1)
state<=s1;
else
state<=s2;
end
s2:begin dout<=0;
if(din==1)
state<=s3;
else
state<=s2;
end
s3:begin dout<=0;
if(din==1)
state<=s4;
else
state<=s2;
end
s4:begin dout<=1;
if(din==1)
state<=s1;
else
state<=s0;
end
default:begin dout<=0;state<=s0;end
endcase
end
end
endmodule

```

### **testbench.sv**

```

module moore_1011_non_overLAP_test;
reg din, reset, clock;
wire dout;
moore_1011_non_overLAP m1(dout,din,clock,reset);
always #10 clock=!clock;
initial begin
$dumpfile("dump.vcd"); $dumpvars;
clock=0;
reset=1;
din=1;
#20 reset=0;din=0;
#20 din=1;

```



```

#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=0;
end
endmodule

```

## **Mealy machine**

### **Overlap method**

#### **Design.sv**

```

module mealey_overlap_1101( output dout, input din,reset, clock);
reg dout;
reg [1:0] state;
parameter S0=2'b00, S1=2'b01, S2=2'b10,S3=2'b11;
always @(posedge clock or posedge reset) begin
if(reset) begin
dout<= 0;
state<= S0;
end
else begin
case(state)
S0: begin
if(din==1)
state<=S1;
else
state<=S0;
dout<=0;
end
S1: begin if(din)
state<=S2;
else
state<=S0;
dout<=0;
end
S2: begin if(din)
state<=S2;
else
state<=S3;
dout<= 0;

```

```

end
S3: begin if(din) begin
state<=S1; dout<=1; end
else begin
state<=S0; dout<=0; end
end
endcase
end
end
endmodule

```

### **Testbench.sv**

```

module mealey_overlap_1101_test;
reg din,reset, clock;
wire dout;
mealey_overlap_1101 m1(dout, din,reset, clock);
always #10 clock =!clock;
initial begin
$dumpfile("dump.vcd"); $dumpvars;
clock=0;
reset=1;
din=1;
#20 reset = 0; din = 1;
#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=0;
end
endmodule

```

## **Non-overlap Method**

### **Design.sv**

```

module mealey_non_overlap_1101( output dout, input din,reset, clock);
reg dout;
reg [1:0] state;
parameter S0=2'b00, S1=2'b01, S2=2'b10,S3=2'b11;
always @(posedge clock or posedge reset) begin
if(reset) begin
dout<= 0;

```



```

state<= S0;
end
else begin
case(state)
S0: begin
if(din==1)
state<=S1;
else
state<=S0;
dout<=0;
end
S1: begin if(din)
state<=S2;
else
state<=S0;
dout<=0;
end
S2: begin if(din)
state<=S2;
else
state<=S3;
dout<= 0;
end
S3: begin if(din) begin
state<=S0; dout<=1; end
else begin
state<=S0; dout<=0; end
end
endcase
end
end
endmodule

```

### **Testbench.sv**

```

module mealey_non_overlap_1101_test;
reg din,reset, clock;
wire dout;
mealey_non_overlap_1101 m1(dout, din,reset, clock);
always #10 clock =!clock;
initial begin
$dumpfile("dump.vcd"); $dumpvars;
clock=0;
reset=1;
din=1;
#20 reset = 0; din = 1;
#20 din=0;
#20 din=1;
#20 din=1;

```

```
#20 din=0;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=1;
#20 din=0;
#20 din=1;
#20 din=0;
end
endmodule
```




# Results




*Fig 5.1 Moore machine in overlap method*



*Fig 5.2: Moore machine in non-overlap method*

 

*Fig 5.3: Mealy machine overlap method*

 

*Fig 5.4: Mealy machine non-overlap method*

Conclusion : In this experiment we learned about Finite state machines and we designed sequence detectors using mealy as well as Moore models for overlapping & non-overlapping sequences by writing codes in EDA playground and simulated them by writing their respective test bench codes to get outputs.